
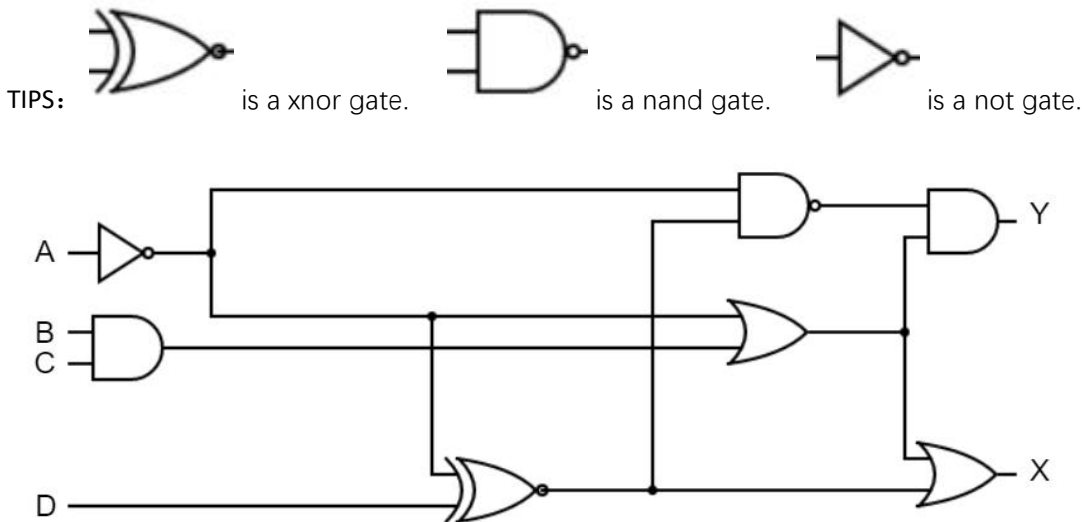


 P1. Use **the logic gates in Verilog** to describe the following circuit in a **structured manner**: the bit width of the four input ports **A**, **B**, **C**, and **D**, as well as the two output ports **X** and **Y**, are all 1 bit. The module name is **lab\_a1\_p1**. (Please note that **keywords such as “assign” and “always” cannot appear in the submitted code**) (10points)



P2. Use **the data flow method in Verilog** to describe the following circuit. The bit widths of the four input ports **A**, **B**, **C**, and **D**, as well as the two output ports **X** and **Y**, are all 1 bit. The module name is **lab\_a1\_p2**. (Please note that logic gates **not**, **and**, **or**, **nor**, **nand**, **xnor**, etc. cannot appear in the submitted code) (10points)



P3. **Build** a testbench to simulate and test the reference circuits, and the modules being tested is named **lab\_a1\_p1**, **lab\_a1\_p2**. (10points)

- Both lab\_a1\_p1 and lab\_a1\_p2 have four input ports A, B, C, D, and two output ports X and Y. The bit widths of A, B, C, D, X and Y, are all 1 bit.
- a\_tb in the testbench connects to port **A** of lab\_a1\_p1 and lab\_a1\_p2;
- b\_tb in the testbench connects to port **B** of lab\_a1\_p1 and lab\_a1\_p2;
- c\_tb in the testbench connects to port **C** of lab\_a1\_p1 and lab\_a1\_p2;
- d\_tb in the testbench connects to port **D** of lab\_a1\_p1 and lab\_a1\_p2.
- x\_tb1 in the testbench connects to port **X** of lab\_a1\_p1;
- x\_tb2 in the testbench connects to port **X** of lab\_a1\_p2;
- y\_tb1 in the testbench connects to port **Y** of lab\_a1\_p1;
- y\_tb2 in the testbench connects to port **Y** of lab\_a1\_p2;

**NOTE:** The simulation time does not exceed 160ns. While submit your code to Verilog-OJ. Please use the **monitor** statement once in initial block (there is only one initial block). For example:

**Initial begin** // just for reference

```
$monitor ("%d %d %d %d %d %d %d %d", a_tb, b_tb, c_tb, d_tb, x_tb1, x_tb2, y_tb1, y_tb2);
```

```
{a_tb, b_tb, c_tb, d_tb} = 4'b0000;
```

```
repeat(15) #10 {a_tb, b_tb, c_tb, d_tb} = {a_tb, b_tb, c_tb, d_tb} + 1;
```

```
#10 $finish;
```

```
end
```

**Tips:** while run the simulation on the testbench, the expected waveform is like: ( the value of {a\_tb,b\_tb,c\_tb,d\_tb} changes from 4'b0000 to 4'b1111 with a step value of 1 for growth)



P4. Use the **logic gates** in Verilog to describe the following conversion circuit in a structured manner. The module name of this circuit is **xb2yg**, the bit width of both its input port **xb** and its output port **yg** are all 4. The circuit converts **xb** into **yg** according to the following table and method.

(Please note that **keywords** such as “**assign**” and “**always**” cannot appear in the submitted code) (10points)

| Group1<br>Input:<br><b>xb</b> | Group1<br>Output:<br><b>yg</b> | Group2<br>Input:<br><b>xb</b> | Group2<br>Output:<br><b>yg</b> | Group3<br>Input:<br><b>xb</b> | Group3<br>Output:<br><b>yg</b> | Group4<br>Input:<br><b>xb</b> | Group4<br>Output:<br><b>yg</b> |
|-------------------------------|--------------------------------|-------------------------------|--------------------------------|-------------------------------|--------------------------------|-------------------------------|--------------------------------|
| 0000                          | 0000                           | 0001                          | 0001                           | 0010                          | 0011                           | 0011                          | 0010                           |
| 0100                          | 0110                           | 0101                          | 0111                           | 0110                          | 0101                           | 0111                          | 0100                           |
| 1000                          | 1100                           | 1001                          | 1101                           | 1010                          | 1111                           | 1011                          | 1110                           |
| 1100                          | 1010                           | 1101                          | 1011                           | 1110                          | 1001                           | 1111                          | 1000                           |

The conversion method is:

1. The **highest bit** of output **yg** is the same as the highest bit of input **xb**; (Tips: Gate buf could keep output and input the same).

2. The calculation method for **other bits of output yg** is as follows:

**yg [i]=xb [i] ^ xb [i+1]** here “^” is **XOR** processing.

For example:

**xb** is 4'b 0100: xb[3] = 1'b0, xb[2] = 1'b1, xb[1] = 1'b0, xb[0] = 1'b0;

yg[3] = xb[3] = 1'b0;

yg[2] = xb[2] ^ xb[3] = 1'b1 ^ 1'b0 = 1'b1;

yg[1] = xb[1] ^ xb[2] = 1'b0 ^ 1'b1 = 1'b1;

yg[0] = xb[0] ^ xb[1] = 1'b0 ^ 1'b0 = 1'b0;

so, while **xb** is 4'b0100, **yg** is 4'b0110.

P5. Use the **data flow** method in Verilog to describe the following conversion circuit. The module name of this circuit is **yg2xb**, the bit width of both its input port **yg** and its output port **xb** are all 4. The circuit converts **yg** into **xb** according to the following table and method.

(Please note that logic gates **not**, **and**, **or**, **nor**, **nand**, **xnor**, etc. cannot appear in the submitted code) (10points)

| Group1<br>input:<br><b>yg</b> | Group1<br>output:<br><b>xb</b> | Group2<br>input:<br><b>yg</b> | Group2<br>output:<br><b>xb</b> | Group3<br>input:<br><b>yg</b> | Group3<br>Output:<br><b>xb</b> | Group4<br>input:<br><b>yg</b> | Group4<br>Output:<br><b>xb</b> |
|-------------------------------|--------------------------------|-------------------------------|--------------------------------|-------------------------------|--------------------------------|-------------------------------|--------------------------------|
| 0000                          | 0000                           | 0001                          | 0001                           | 0011                          | 0010                           | 0010                          | 0011                           |
| 0110                          | 0100                           | 0111                          | 0101                           | 0101                          | 0110                           | 0100                          | 0111                           |
| 1100                          | 1000                           | 1101                          | 1001                           | 1111                          | 1010                           | 1110                          | 1011                           |
| 1010                          | 1100                           | 1011                          | 1101                           | 1001                          | 1110                           | 1000                          | 1111                           |

The conversion method is:

1. The highest bit of output **xb** is the same as the highest bit of input **yg**;
2. The calculation method for **other bits of output xb** is as follows:

**xb [i]=yg [i] ^ xb [i+1]** here “^” is **XOR** processing

For example:

yg is **4'b 0110**: yg[3] = 1'b0, yg[2] = 1'b1, yg[1] = 1'b1, yg[0] = 1'b0;

xb[3] = yg[3] = 1'b0;

xb[2] = yg[2] ^ xb[3] = 1'b1 ^ 1'b0 = 1'b1;

xb[1] = yg[1] ^ xb[2] = 1'b1 ^ 1'b1 = 1'b0;

xb[0] = yg[0] ^ xb[1] = 1'b0 ^ 1'b0 = 1'b0;

so, while **yg** is **4'b0110**, **xb** is **4'b0100**.

P6. Build a testbench to simulate and test the reference circuits, and the modules being tested is named **xb2yg**, **yg2xb**. (10points)

- The bitwidth of both **xb2yg**'s input port **xb** and its output port **yg** are all 4.
- The bitwidth of both **yg2xb**'s input port **yg** and its output port **xb** are all 4.
- **in\_tb** in the testbench connects to port **xb** of **xb2yg** and port **yg** of **yg2xb**;
- **out\_xb2yg** in the testbench connects to port **yg** of **xb2yg**;
- **out\_yg2xb** in the testbench connects to port **xb** of **yg2xb**;

NOTE: The simulation time does not exceed 160ns. While submit your code to Verilog-OJ, please use the monitor statement once in **initial** block (there is only one **initial** block). For example


**Initial begin**

```
$monitor ("% d % d % d%", in_tb, out_xb2yg, out_yg2xb);
```

```
// your code here
```

**end**

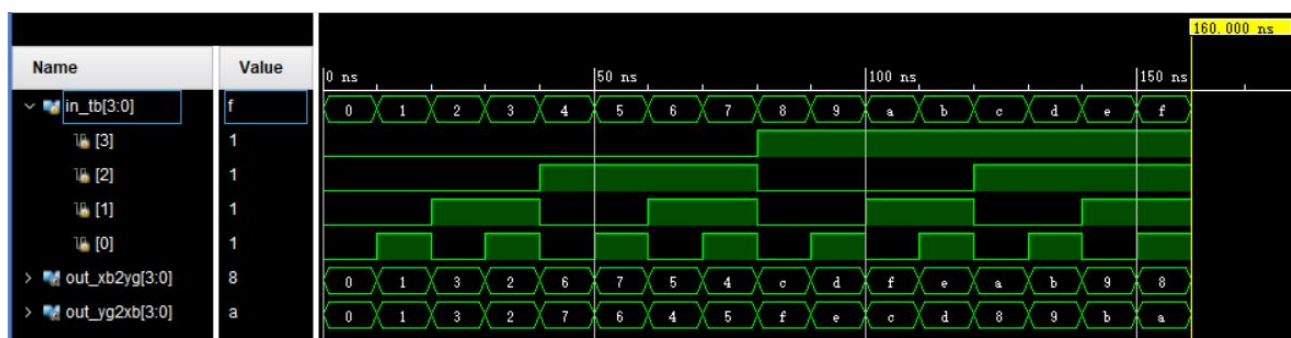**Tips: while run the simulation on the testbench, the expected waveform is like: ( the value of in\_tb changes from 4'b0000 to 4'b1111 with a step value of 1 for growth)**



P7. Design a circuit to get the addition of two two-bit unsigned numbers. The inputs are **a** and **b** which are both 2 bits, the output is **sum** which is 3 bits. (10points)


The truth table of the circuit is:

| a[1] | a[0] | b[1] | b[0] | sum[2] | sum[1] | sum[0] |
|------|------|------|------|--------|--------|--------|
| 0    | 0    | 0    | 0    | 0      | 0      | 0      |
| 0    | 0    | 0    | 1    | 0      | 0      | 1      |
| 0    | 0    | 1    | 0    | 0      | 1      | 0      |
| 0    | 0    | 1    | 1    | 0      | 1      | 1      |
| 0    | 1    | 0    | 0    | 0      | 0      | 1      |
| 0    | 1    | 0    | 1    | 0      | 1      | 0      |
| 0    | 1    | 1    | 0    | 0      | 1      | 1      |
| 0    | 1    | 1    | 1    | 1      | 0      | 0      |
| 1    | 0    | 0    | 0    | 0      | 1      | 0      |
| 1    | 0    | 0    | 1    | 0      | 1      | 1      |
| 1    | 0    | 1    | 0    | 1      | 0      | 0      |
| 1    | 0    | 1    | 1    | 1      | 0      | 1      |
| 1    | 1    | 0    | 0    | 0      | 1      | 1      |
| 1    | 1    | 0    | 1    | 1      | 0      | 0      |
| 1    | 1    | 1    | 0    | 1      | 0      | 1      |
| 1    | 1    | 1    | 1    | 1      | 1      | 0      |

 **NOTE: In the design, the operator + in verilog is NOT allowed here.**

A testbench is built to verify the function of the circuit **lab3\_practic\_add2bit**: **a\_tb** is a reg which connects to port **a**, **b\_tb** is a reg which connects to port **b**, **sum\_tb** is a wire which connects to port **sum**.

The expected waveform of the testbench which verify the function of the circuit **lab3\_practic\_add2bit** is as following picture:




P8. Build a testbench to test the circuit **lab3\_practic\_add2bit**. (10points)

The function of the circuit **lab3\_practic\_add2bit** is to get the addition of two two-bit unsigned numbers. Its inputs are **a** and **b** which are both 2 bits, its output is “sum” which is 3 bits:

It is asked to build a **testbench** to verify the function of the circuit **lab3\_practic\_add2bit**:

- **a\_tb** in the testbench connects to port **a** of **lab3\_practic\_add2bit**
- **b\_tb** in the testbench connects to port **b** of **lab3\_practic\_add2bit**
- **sum\_tb** in the testbench connects to port **sum** of **lab3\_practic\_add2bit**

 The expected waveform of the testbench which verify the function of the circuit **lab3\_practic\_add2bit** is as following picture:



NOTE: The simulation time does not exceed 160ns. While submit your code to Verilog-OJ, please use the monitor statement once in initial block (there is only one initial block). For example

**Initial begin**


```
$monitor("%d %d %d", a_tb, b_tb, sum_tb);
```

```
// your code here
```

**end**

P9: Please finish the test "lab\_assignment1\_part1" in the course sit on BlackBoard. (20points)

"Tests" → "lab\_assignment1\_part1"

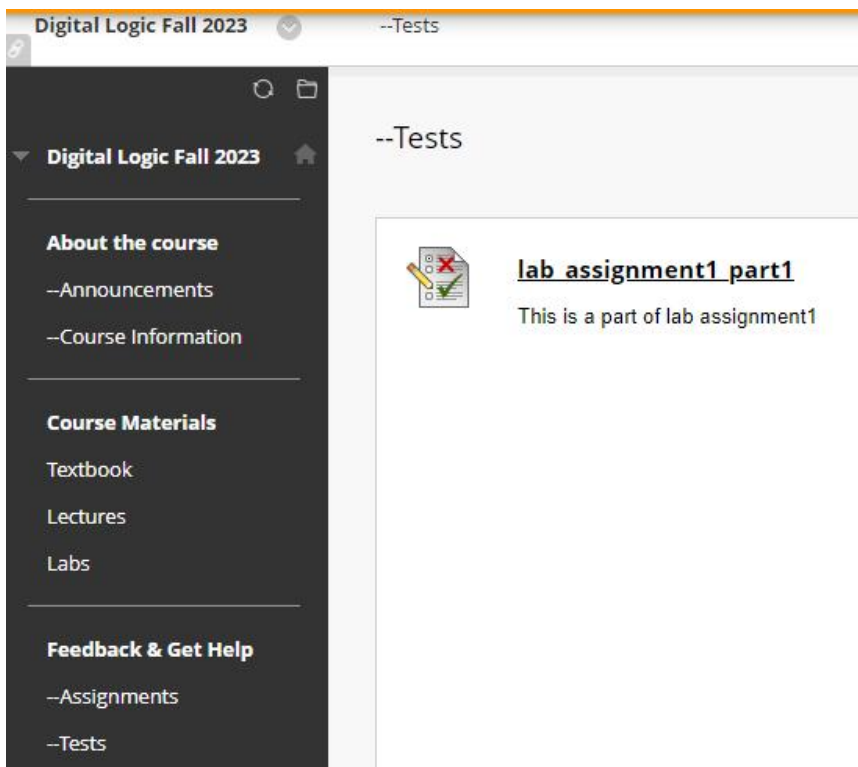

There are 10 attempts for your submission, the blackboard would record the Highest grade.

☒ Multiple Attempts

☐ Allow Unlimited Attempts

☒ Number of Attempts 10

Score attempts using

Highest Grade