

Assignment 4

1. We need 4 DFF, suppose they're A_3, A_2, A_1, A_0 .

Analyze the 4x1 mux connected to A_3 as an example.


When $S_1S_0 = 00$, means no change, so A_3 should connect to port 0.

Similarly, $S_1S_0 = 01$, A_3 should be input into port 1.

$S_1S_0 = 10$, 0 should be input of port 2.

And $S_1S_0 = 11$, means parallel input, I_3 should connect to 3.


We can draw the diagram.

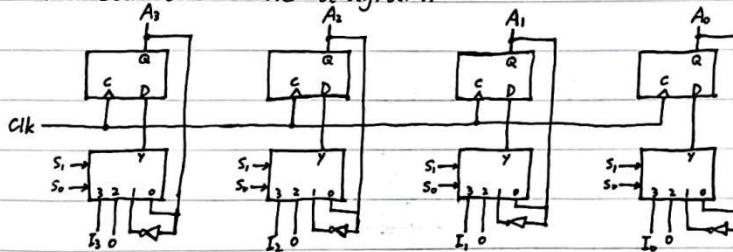

2. $\text{length}(1011110) = 7 \leq 2^3 - 1$, we should use at least 3 FF (choose DFF for easy). But in first 3 DFF, there're repeat state, so we add one DFF.


clk	Z	Q_3	Q_2	Q_1	Q_0
↑	0	1	0	1	1
↑	1	0	1	0	1
↑	1	1	0	1	0
↑	1	1	1	0	1
↑	1	1	1	1	0
↑	0	1	1	1	1
↑	1	0	1	1	1

Then we draw K-map of Z:

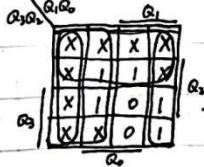

$$Z = Q_3' + Q_0' + Q_1'$$

At last, draw diagram:

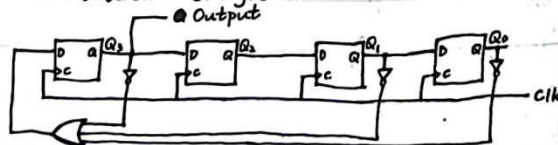



No.

Date

3. Use 4 DFF to design. The state table is as follow.



Present State				Next State (DFF input)			
A	B	C	D	A(D _A)	B(D _B)	C(D _C)	D(D _D)
0	0	0	0	0	0	1	0
0	0	0	1	0	0	1	0
0	0	1	0	0	1	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	0	1	0
0	1	0	1	0	0	1	0
0	1	1	0	1	0	0	1
0	1	1	1	0	0	1	0
1	0	0	0	1	1	0	0
1	0	0	1	1	0	0	0
1	0	1	0	0	0	1	0
1	0	1	1	0	0	1	0
1	1	0	0	1	1	0	1
1	1	0	1	0	0	1	0
1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0

Use K-map get 4 DFFs' input equation:

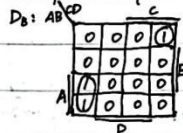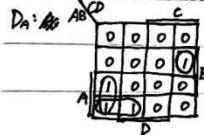


$$D_A = AC'D + AB'C' + A'BCD'$$

$$D_B = AC'D + A'B'CD'$$

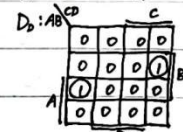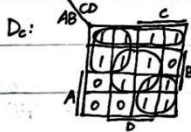

$$D_C = A'B' + A'C' + BD + AC$$

$$D_D = ABC'D' + A'BCD'$$

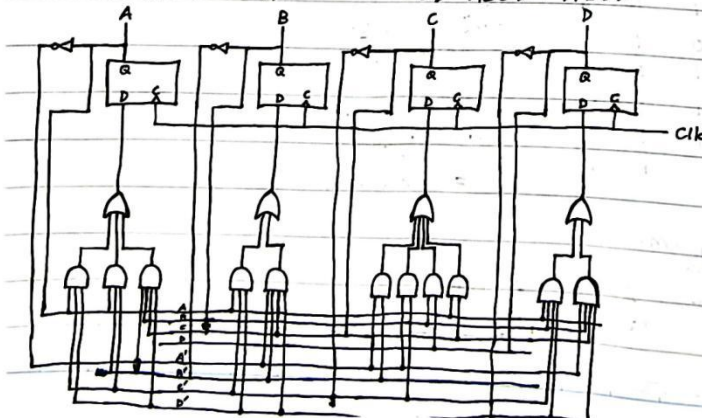

But we can also use only 3 DFFs to do the design.


Suppose 8 states: 000 (output 0010), 001 (output 0110), 010 (output 1001),

011 (output 1000), 100 (output 1100), 101 (output 1101), 110 (output don't care),

111 (output don't care). State 110, 111 must go to state 000.

Present state			Next State (DFF input)			Output			
L	M	N	D _L	D _M	D _N	A	B	C	D
0	0	0	0	0	1	0	0	1	0
0	0	1	0	1	0	0	1	1	0
0	1	0	0	1	1	1	0	0	1
0	1	1	1	0	0	1	0	0	0
1	0	0	1	0	1	1	1	0	0
1	0	1	0	0	0	1	1	0	1
1	1	0	0	0	0	x	x	x	x
1	1	1	0	0	0	x	x	x	x

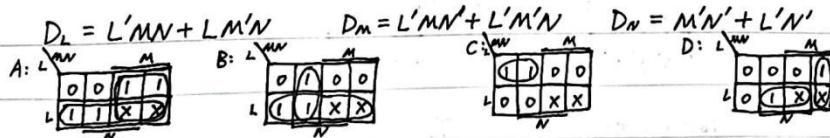Use K-map to get DFFs' input equation and output combination logic.




$$A = M + L$$


$$B = L + M'N$$

$$C = L'M'$$

$$D = LN + MN'$$



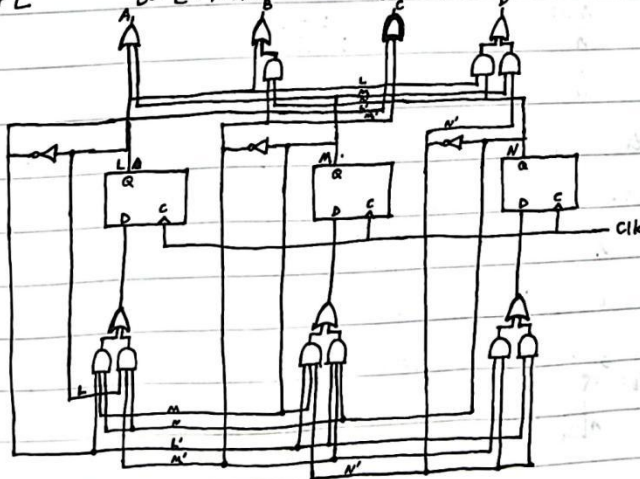


4. The state machine like below.

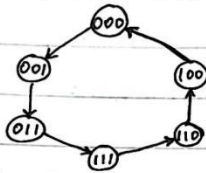

Use 3 TFFs to design (suppose they're A, B, C)

Present state			Next state			TFF input		
A	B	C	A	B	C	T_A	T_B	T_C
0	0	0	0	0	1	0	0	1
0	0	1	0	1	1	0	1	0
0	1	0	X	X	X	X	X	X
0	1	1	1	1	1	1	0	0
1	0	0	0	0	0	1	0	0
1	0	1	X	X	X	X	X	X
1	1	0	1	0	0	0	1	0
1	1	1	1	1	0	0	0	1

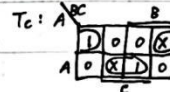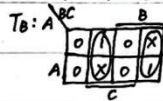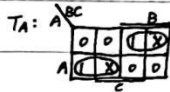

$$T_A = A'B + AB'$$

$$T_B = B'C + BC'$$

$$T_C = AC + A'C'$$




Then, the 'X' in state table is like this.

Present state			Next state			TFF input		
A	B	C	A	B	C	T_A	T_B	T_C
0	1	0	1	0	1	1	1	1
1	0	1	0	1	0	1	1	1

The extra 2 states will occur a lock out, so we correct the design by make 010 and 101 next state to 000.

Present state			Next state			TFF input		
A	B	C	A	B	C	T_A	T_B	T_C
0	1	0	0	0	0	0	1	0
1	0	1	0	0	0	1	0	1

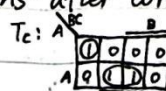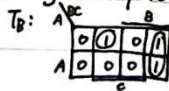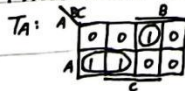Then used K-map to get input equations after correct the design.



$$T_A = AB' + A'BC$$

$$T_B = A'BC' + BC'$$

$$T_C = A'B'C' + AC$$

The block diagram:

