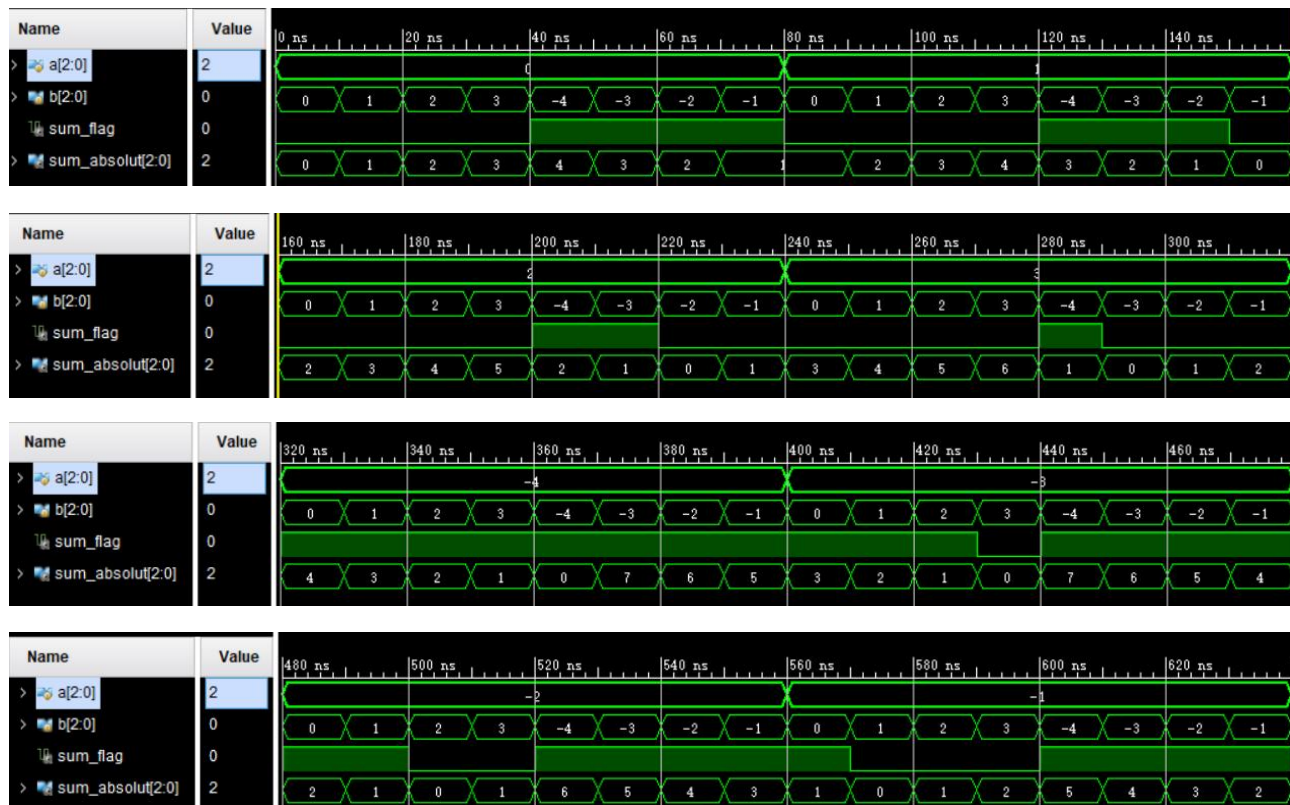


Lab_assignment2

Digital_Design_2023_fallterm@cse.sustech

P1. use **Verilog** to describe the following circuit: the module name is **lab_a2_p1**, with 2 input port **a** and **b**, the bit-width of both **a** and **b** is **3**, the circuit treat **a** and **b** as **signed number** and do the **signed addition operation** on them, there are 2 **output** ports of lab_a2_p1: **sum_flag** and **sum_absolut**. The bit-width of **sum_flag** is 1. If the sum of a and b is ≥ 0 , then **sum_flag** is **1'b0**, otherwise, **sum_flag** is **1'b1**. The bit-width of **sum_absolut** is 3, it is the absolute value of the sum of a and b.(10points)

Tips: while run the simulation on the testbench to test the circuit, the expected waveform is like:



P2. Build a testbench to simulate and test the reference circuits, and the modules being tested is named **lab_a2_p1**. (10points)

- **lab_a2_p1** have 2 input ports **a**, **b** and two output ports **sum_flag** and **sum_absolut**. The bit widths of a,b and sum_absolut are all 3, The bit width of sum_flag is 1.
- **a** in the testbench connects to port **a** of **lab_a2_p1**;
- **b** in the testbench connects to port **b** of **lab_a2_p1**;
- **sum_flag** in the testbench connects to port **sum_flag** of **lab_a2_p1**;
- **sum_absolut** in the testbench connects to port **sum_absolut** of **lab_a2_p1**;

NOTE: Before submitting your code to Verilog-OJ, please make sure to use the **monitor** statement only once in initial block (there is only one initial block). For example:

Initial begin // just for reference

\$monitor ("%d %d %d %d", a, b, sum_flag, sum_absolut);

{a,b} = 6'b000_000;

repeat (/*to be complete*/) **#10 {a,b} = {a,b} + 1;**

#10 \$finish;

end

Tips: The expected waveform are like the pictures of P1 while running the simulation on the testbench,

P3. Design a circuit which get the addition of two three-bit signed numbers, and display the decimal

representation of the result on the two 7-segment tubes, assuming the two 7-segment tubes' name are: **tub_sflag** and **tub_sabsolut**. (10points)

The name of 7-segment tubes	It's tub_select (1bit) While it's 1 means tube work, otherwise means not wok	It's tub_control (8bit)
tub_sflag	tub_sflag_sel	tub_sflag_control
tub_sabsolut	tub_sabsolut_sel	tub_sabsolut_control

The module name is **lab_a2_p3**, with 2 input ports **a** and **b**, 4 output ports **tub_sflag_sel**, **tub_sabsolut_sel**, **tub_sflag_control** and **tub_sabsolut_control**. The bit-width of **a** and **b** is 3, the bit-width of **tub_sflag_sel** and **tub_sabsolut_sel** is 1, the bit-width of **tub_sflag_control** and **tub_sabsolut_control** is 8.

- ✓ If the sum of **a** and **b** is negative, both two 7-segment tube work, that means the value of both **tub_sflag_sel** and **tub_sabsolut_sel** are 1'b1, **tub_sflag** display the charactor "-", **tub_sabsolut** display the absolute value of sum in decimal.
- ✓ If the sum of **a** and **b** is not negative, **tub_sflag** don't work, that means **tub_sflag_sel** is 1'b0, only **tub_sabsolut** work which means **tub_sabsolut_sel** is 1'b1, **tub_sabsolut** display the absolute value of sum in decimal.

NOTE: It is asked to use module **lab_a2_p1** and **lab_a2_p3_tub_display** to do the circuit design in **structural manner**. Both these two modules are provided on the OJ, the definition of **lab_a2_p1** is exactly same as the module **lab_a2_p1** of this assignment, the definition of **lab_a2_p3_tub_display** is as the content in the following table.


```



module lab_a2_p3_tub_display(
input [3:0] in_b4, input tub_sel_in, output tub_sel_out, output reg [7:0] tub_control );

    assign tub_sel_out = tub_sel_in;
    //tub_control := {a,b,c,b,e,f,g,"dot"}
    always @ * begin
        case(in_b4)
            4'b0000: tub_control = 8'b1111_1100;    //"0": abcdef__
            4'b0001: tub_control = 8'b0110_0000;    //"1": _bc_____
            4'b0010: tub_control = 8'b1101_1010;    //"2": ab_de_g_
            4'b0011: tub_control = 8'b1111_0010;    //"3": abcd__g_
            4'b0100: tub_control = 8'b0110_0110;    //"4": _bc__fg_
            4'b0101: tub_control = 8'b1011_0110;    //"5": a_cd_fg_
            4'b0110: tub_control = 8'b1011_1110;    //"6": a_cdefg_
            4'b0111: tub_control = 8'b1110_0000;    //"7": abc_____
            4'b1000: tub_control = 8'b1111_1110;    //"8": abcdefg_
            4'b1001: tub_control = 8'b1110_0110;    //"9": abc__fg_
            4'b1111: tub_control = 8'b0000_0010;    //" ": _____g_
            default:
                tub_control = 8'b1001_1110;        //"E": a__defg_
        endcase
    end
endmodule

```

 Tips: while run the simulation on the testbench, the expected waveform is like:



  

P4. Build a testbench to simulate and test the design you make in P3, and the modules being tested is named lab_a2_p3. (10points)

- lab_a2_p3 have 2 input ports **a**, **b** and 4 output ports **tub_sflag_sel**, **tub_sflag_control**, **tub_sabosolut_sel**, **tub_sabsolut_control**. The bit widths of a,b are all 3. The bit width of **tub_sflag_sel**, **tub_sabosolut_sel** are all 1. The bit width of **tub_sflag_control**, **tub_sabsolut_control** are all 8.
- **a** in the testbench connects to port **a** of lab_a2_p3;
- **b** in the testbench connects to port **b** of lab_a2_p3;
- **tub_sflag_sel** in the testbench connects to port **tub_sflag_sel** of lab_a2_p3;
- **tub_sflag_control** in the testbench connects to port **tub_sflag_control** of lab_a2_p3;
- **tub_sabosolut_sel** in the testbench connects to port **tub_sabosolut_sel** of lab_a2_p3;
- **tub_sabsolut_control** in the testbench connects to port **tub_sabsolut_control** of lab_a2_p3;

NOTE: Before submitting your code to Verilog-OJ, make sure to use the **monitor** statement only once in initial block.

Tips: while run the simulation on the testbench, the expected waveform are like the pictures of P3.

P5. Design a circuit which calculates the number of 1 in the input signal. If the number of 1 is greater than the number of 0, output 1; otherwise, output 0. (10points)

The module name is **lab_a2_p5**, with 4 input port **a,b,c,d**. The bit-width of both a,b,c and d is **1**. There are **2** output ports which are named **more1_somin** and **more1_pomax**, both of them are **1** bit. While using **Sum of Minterm** to implement the circuit, assign the result to **more1_somin**, while using **Product of Maxterm** to implement the circuit, assign the result to **more1_pomax**.

For example:

more1_somin	more1_pomax	number of 1 in the input:	a,b,c,d				
1	4	4'b1111	..				
1	3	4'b0111	4'b1011	4'b1101	4'b1110	..	
0	2	4'b0011	4'b0101	4'b1001	4'b1100	4'b1010	..
0	1	4'b0001	4'b0010	4'b0100	4'b1000	..	
0	0	4'b0000	..				

NOTE: please using “assign” to implement the circuit, gates and “always” are not allowed in this assignment

P6. Design a circuit which calculate the number of 1 in the input signal. If the number of 1 is greater than the number of 0, output 1. Implement it using **behavior modeling method**. The module name is **lab_a2_p6**, with 1 input port **in** and 1 output port **more1**. The bit-width of **in** is **4**, the bit-width of **more1** is **1**. (10points)

NOTE: “always” block is expected, don’t use any gates or keyword “assign”

P7. Re-implement the design of P6 using **module MUX_16_1** and design in **structural manner**. The module name is **lab_a2_p7**, with 1 input port **in** and 1 output port **more1**. (10points)

NOTE:

keyword “always” and any gates are not allowed in this module, “MUX_16_1” **MUST** be used in your code, the output port **more1** **MUST** connect with the output of the “MUX_16_1”.

TIPS: The module **MUX_16_1** would be provided on the OJ, the definition of **MUX_16_1** is as the content in the following table.

```
module MUX_16_1(input [3:0] sel, input [15:0] data_in, output reg data_out );
    always @ * begin
        case(sel)
            4'b0000: data_out = data_in[0];
            4'b0001: data_out = data_in[1];
            4'b0010: data_out = data_in[2];
            4'b0011: data_out = data_in[3];
            4'b0100: data_out = data_in[4];
            4'b0101: data_out = data_in[5];
            4'b0110: data_out = data_in[6];
            4'b0111: data_out = data_in[7];
            4'b1000: data_out = data_in[8];
            4'b1001: data_out = data_in[9];
            4'b1010: data_out = data_in[10];
            4'b1011: data_out = data_in[11];
            4'b1100: data_out = data_in[12];
            4'b1101: data_out = data_in[13];
            4'b1110: data_out = data_in[14];
            4'b1111: data_out = data_in[15];
        endcase
    end
endmodule
```

P8. Re-implement the design of P6 using **module MUX_8_1** and design in **structural manner**. The module name is **lab_a2_p8**, with 1 input port **in** and 1 output port **more1**. (10points)

NOTE: keyword “always” and any gates are not allowed in this module, “MUX_8_1” **MUST** be used in your code, the output port **more1** **MUST** connect with the output of the “MUX_8_1”.

TIPS: The module **MUX_8_1** would be provided on the OJ, the definition of **MUX_8_1** is as the content in the following table.

```
module MUX_8_1( input [2:0] sel, input [7:0] data_in, output reg data_out );
    always@* begin
        case(sel)
            3'b000: data_out = data_in[0];
            3'b001: data_out = data_in[1];
            3'b010: data_out = data_in[2];
            3'b011: data_out = data_in[3];
            3'b100: data_out = data_in[4];
```

```

    3'b101: data_out = data_in[5];
    3'b110: data_out = data_in[6];
    3'b111: data_out = data_in[7];
endcase
end
endmodule

```

P9: Re-implement the design of P6 using module **Decoder_4_16** and design in **structural manner** The module name is **lab_a2_p9**, with 1 input port **in** and 1 output port **more1**. (10points)

NOTE: keyword “always”, “assign” are **NOT** allowed in this module. “Decoder_4_16” and “or”gate **MUST** be used in your code, the output port **more1** **MUST** connect with the output of the “or” gate.

TIPS: The module **Decoder_4_16** would be provided on the OJ, the definition of **Decoder_4_16** is as the content in the following table.

```

module Decoder_4_16( input [3:0] in, output reg [15:0] out );
  always@* begin
    case(in)
      4'b0000: out = 16'h0001;
      4'b0001: out = 16'h0002;
      4'b0010: out = 16'h0004;
      4'b0011: out = 16'h0008;
      4'b0100: out = 16'h0010;
      4'b0101: out = 16'h0020;
      4'b0110: out = 16'h0040;
      4'b0111: out = 16'h0080;
      4'b1000: out = 16'h0100;
      4'b1001: out = 16'h0200;
      4'b1010: out = 16'h0400;
      4'b1011: out = 16'h0800;
      4'b1100: out = 16'h1000;
      4'b1101: out = 16'h2000;
      4'b1110: out = 16'h4000;
      4'b1111: out = 16'h8000;
    endcase
  end
endmodule

```

P10: Build a testbench to simulate and test the circuits from p5 to p9, and the modules being tested is named **lab_a2_p5, lab_a2_p6, lab_a2_p7, lab_a2_p8, lab_a2_p9**. (10points)

- The bit-width of the input port of both **lab_a2_p5, lab_a2_p6, lab_a2_p7, lab_a2_p8** and **lab_a2_p9** are 4, The bit-width of output port **more1** of both **lab_a2_p6, lab_a2_p7, lab_a2_p8** and **lab_a2_p9** are 1 bit, the bit-width of output port **a2_p5_somin** and **a2_p5_pomax** are 1.
- **in** in the testbench connects to port **a,b,c,d** of **lab_a2_p5, lab_a2_p6,lab_a2_p7, lab_a2_p8, lab_a2_p9** ;
- **a2_p5_somin** in the testbench connects to port **more1_somin** of **lab_a2_p5**;
- **a2_p5_pomax** in the testbench connects to port **more1_pomax** of **lab_a2_p5**;
- **a2_p6_more1** in the testbench connects to port **more1** of **lab_a2_p6**;
- **a2_p7_more1** in the testbench connects to port **more1** of **lab_a2_p7**;
- **a2_p8_more1** in the testbench connects to port **more1** of **lab_a2_p8**;
- **a2_p9_more1** in the testbench connects to port **more1** of **lab_a2_p9**;

NOTE: Before submitting your code to Verilog-OJ, please make sure to use the **monitor** statement once in initial block (there is only one initial block).

Tips: while run the simulation on the testbench, the expected waveform is like:

